

Memorandum

Q1.

$$1.1 \quad P = VI \quad \therefore I = \frac{P}{V} = \frac{18W}{220V} (A) = \frac{18000}{220} mA$$

$$= 81.82 mA$$

Answer B

1.2

$$R_{AB} = 1K \parallel (2K \parallel 3K)$$

$$= 1K \parallel \left(\frac{2 \times 3}{2+3} \right) K$$

$$= 1K \parallel \frac{6}{5} K$$


$$= \frac{1 \times \frac{6}{5}}{1 + \frac{6}{5}} = \frac{\frac{6}{5}}{\frac{11}{5}} K$$

$$= \frac{6}{11} K \quad \text{or} \quad \frac{6000}{11} \Omega$$

$$= 545.45 \Omega$$

Answer D

1.3

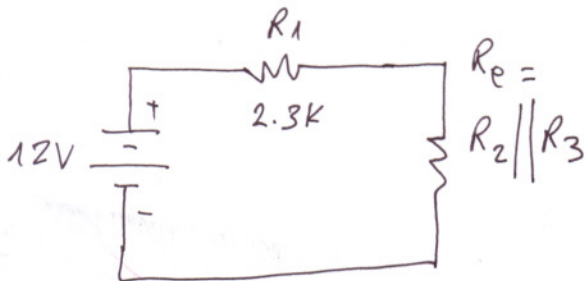

$$R_e = \frac{R_2 R_3}{R_2 + R_3} = \frac{5.6(8.9)}{5.6 + 8.9} K$$

Answer D

⇒ Potential Divider

$$\approx 3.437K$$

$$\therefore V_e = \left(\frac{R_e}{R_1 + R_e} \right) 12 = \frac{3.437}{2.3 + 3.437} \times 12 = 7.189V \approx 7.2V$$

1.4

Transformer is step-up

$$\begin{aligned} \Rightarrow V_{AB} = V_s &= nV_p \\ &= \frac{2}{1} * 120V_{rms} \\ &= \underline{240V_{rms}} \Rightarrow \underline{\text{Answer D}} \\ \text{or } 240\sqrt{2} V_{pk} \\ &= \underline{339.41V_{pk}} \end{aligned}$$

1.5

Zener diode is forward biased

\Rightarrow Ordinary diode

i.e. $V_Z = V_D = 0.7V$

\therefore KVL around the loop gives

$$\begin{aligned} -12 + IR_1 + V_Z &= 0 \\ \Rightarrow -12 + 2I + 0.7 &= 0 \\ \therefore I &= \frac{12 - 0.7}{2} \text{ mA} \\ &= \underline{\underline{5.65 \text{ mA}}} \end{aligned}$$

Answer B

1.6

LED is reverse biased \Rightarrow only reverse


saturation current flows $\rightarrow \underline{\underline{0}}$

Answer D

2.1 (i) KVL states that the algebraic sum of (all the) potential differences around a closed-loop in a circuit is zero.

(ii) KCL states that the algebraic sum of currents at a node in a circuit is zero.

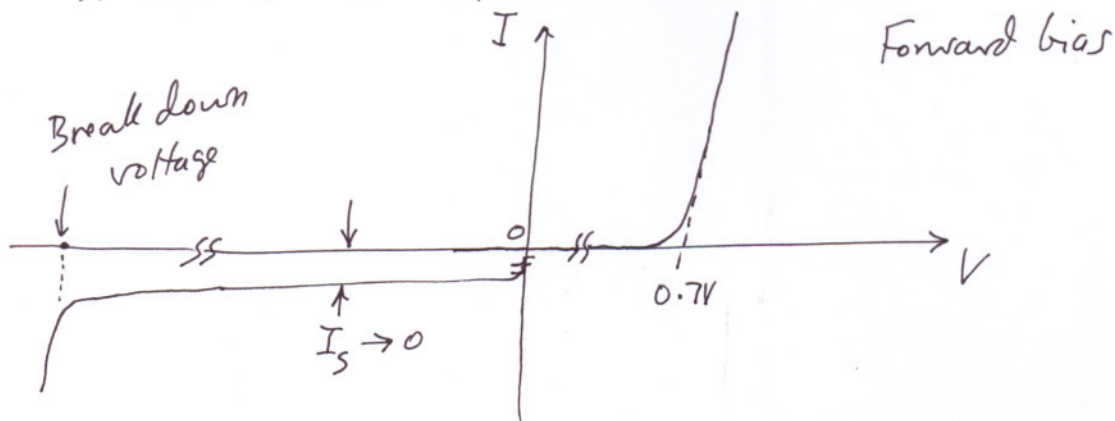2.2 (a) Silicon $\Rightarrow V_D = V_\phi \approx 0.7V$



Reverse bias


I_S = reverse saturation current.

(b) $P_Z = 5Watt$

$V_Z = 5.1V$


$\therefore I_Z = \frac{P_Z}{V_Z} = \frac{5}{5.1} A$

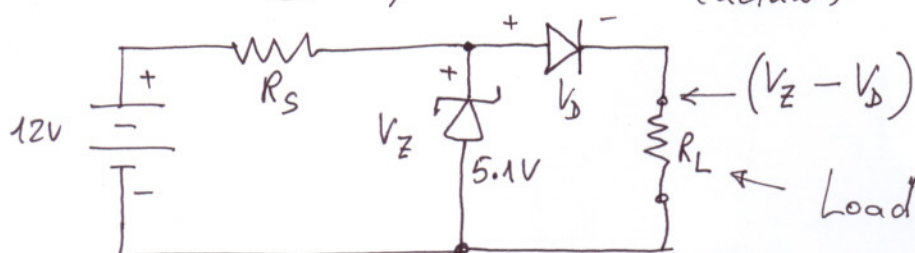Derating by 50% $\Rightarrow I_Z (\text{actual}) = \frac{1}{2} \times \frac{5}{5.1} A = 0.4902 A$



where $V_D = 0.7V$
Refers to a silicon diode's barrier potential.

Value of R_s

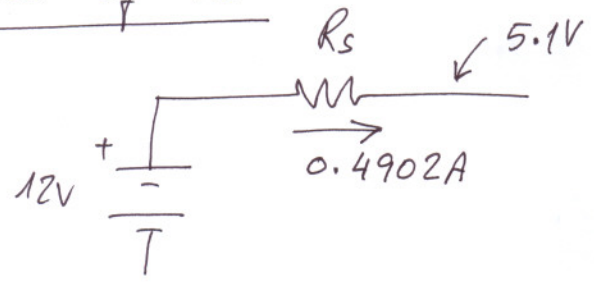

$$R_s = \frac{V_s}{I_s}$$

$$= \frac{12 - 5.1}{0.4902} \frac{V}{A} (\Omega)$$

$$= 14.076 \Omega$$

Power dissipation in R_s

is $P_s = V_s I_s$

$$= (12 - 5.1)(0.4902) \text{ Watts}$$

$$= 3.382 \text{ W (minimum required value)}$$

Therefore use at

least 14Ω , 3.38 W tolerant
series resistor

2.3 Single wound \Rightarrow 4 diodes in bridge configuration.
output

$$V_p = 220 V_{rms} / 50 \text{ Hz (South Africa)}$$

$V_o = +12V$ (DC) \Rightarrow use 7812 linear regulator, with at least $2V$ across regulator,

$$\Rightarrow V_{CAP} = 12 + 2 = 14V = V_{pk}.$$

(filter) (min.) (secondary)

Hence filter capacitor must have at least 16 Volt rating.

Factoring in two diode drops, the peak value of V_s is then

$$V_{s(PK)} = V_{CAP} + 2V_D = 14 + 2(0.7) = 15.4V$$

$$V_{s(RMS)} = \frac{V_{s(PK)}}{\sqrt{2}} = \frac{15.4}{\sqrt{2}} V = 10.89V \approx 11V$$

Hence transformer turns ratio is

$$n = \frac{V_p}{V_s} = \frac{220V}{11V} = 20 \text{ (minimum)}$$


Also, it should be able to handle $1A_{pk}$ output

⇒ its power rating (or V-A capacity) is

$$V_{s(RMS)} \times I_{RMS} = 11 \times \frac{1}{\sqrt{2}} VA = 7.8 VA$$


Optional for you
FSK
224
students

CIRCUIT

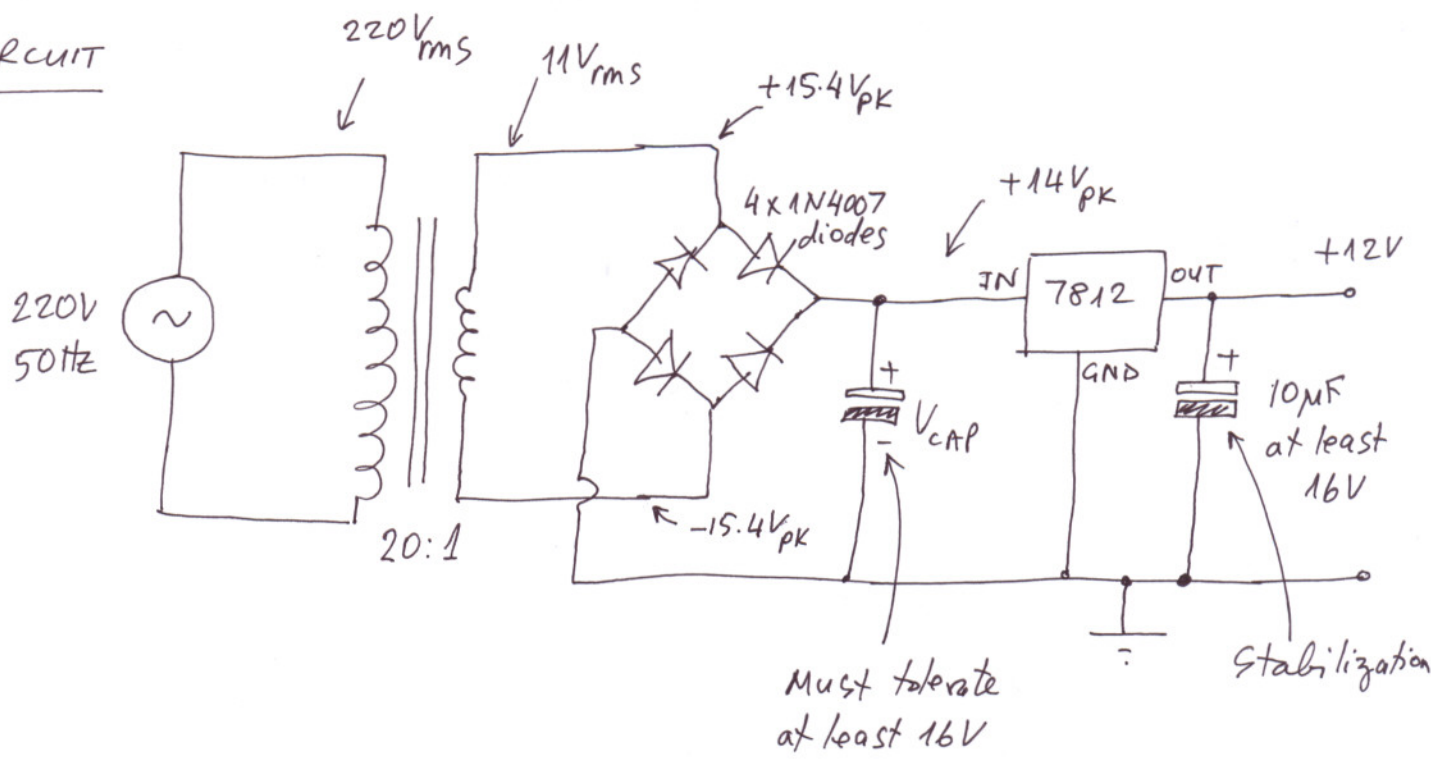

2.3

6

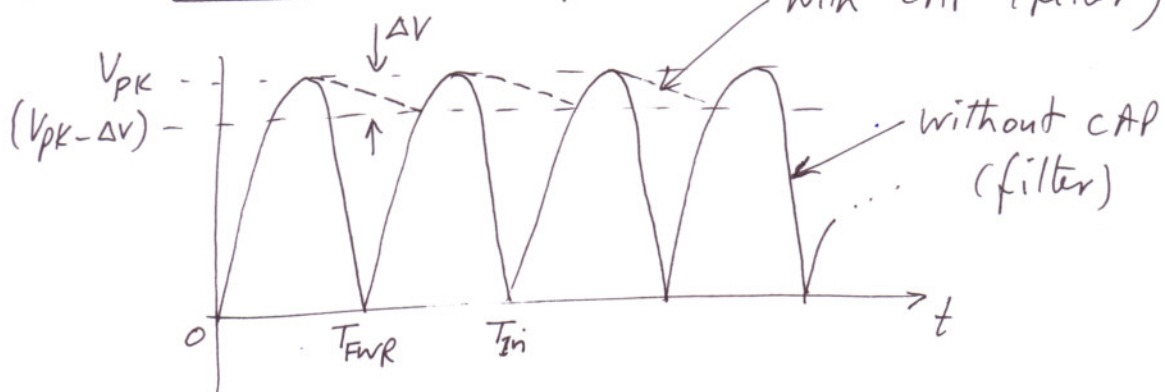(b) Full-wave Rectifier

Assuming ideal diodes

$$\Delta Q = C \Delta V$$

$$I \approx \frac{\Delta Q}{\Delta t} \approx \frac{C \Delta V}{T_{FWR}}$$

where $T_{FWR} = \frac{1}{2} T_{in}$

$$\therefore f_{FWR} = 2 f_{in}$$

$$I = 2 f_{in} C \Delta V$$

$$\text{or } C = \frac{I}{2 f_{in} \Delta V}$$

Note:

$$I = 1A$$

$$\Delta V \approx V_{PK} - V_{CAP (min)}$$

$$f_{in} = 50Hz$$

$$(c) C = 250 \mu F = 250 \cdot 10^{-6} F$$

$$\Delta V = 0.25V$$

$$V = 12V$$

$$f_{in} = 50Hz$$

$$I = \frac{V}{R_L}$$

$$\Rightarrow C = \frac{V}{2 f_{in} R_L \Delta V}$$

$$\Rightarrow R_L = \frac{V}{2 f_{in} C \Delta V}$$



$$= \frac{12}{2(50)(250) \cdot 10^{-6} * 0.25} \Omega$$

$$= 1920 \Omega$$

$$= \underline{\underline{1.92 K \Omega}}$$



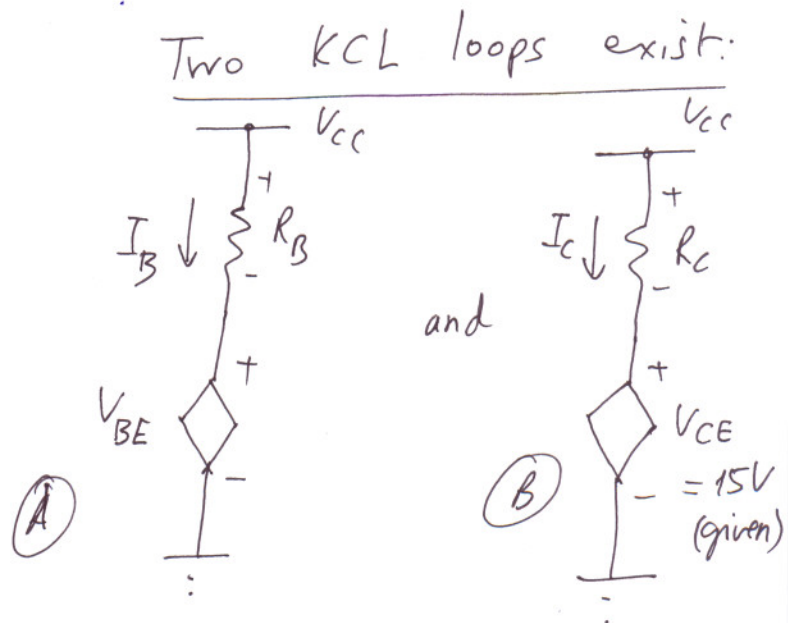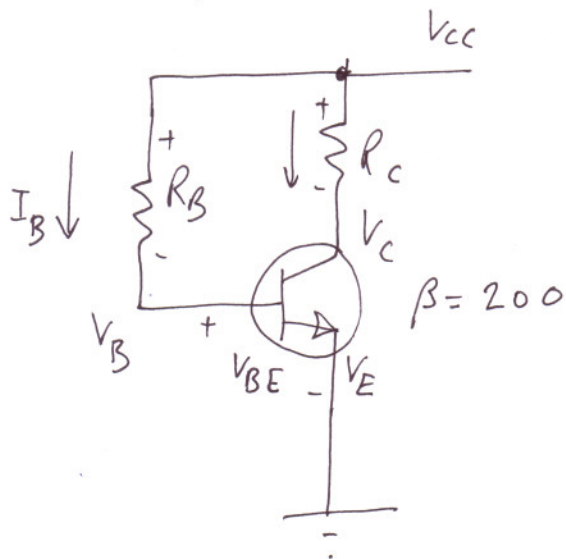2.4 For bias point calculation, eliminate all capacitors. ⑦



Using (A)

$$-V_{CC} + I_B R_B + V_{BE} = 0$$

$$\Rightarrow -30 + I_B R_B + 0.7 = 0 \quad \text{--- (1)}$$

Using (B)

$$-V_{CC} + I_C R_C + V_{CE} = 0 \quad \text{--- (2)}$$

$$\Rightarrow -30 + I_C (2.2) + 15 = 0$$

$$\Rightarrow I_C = \frac{30 - 15}{2.2} \text{ mA} = 6.818 \text{ mA} \quad \text{(or } 6818 \mu\text{A)}$$

$$\therefore I_B = \frac{I_C}{\beta} = \frac{6818}{200}$$

$$= 34.09 \mu\text{A} \quad \text{--- (3)} \quad \text{(or } 0.03409 \text{ mA)}$$

(3) into (1)

$$\Rightarrow R_B = \frac{30 - 0.7}{0.03409} \frac{\text{V}}{\text{mA}} \quad (\text{K}\Omega)$$

$$= 859.47 \text{ K}\Omega$$

$$\underline{R_B \approx 860 \text{ K}\Omega}$$

2.5

$$(a) \quad V_{\text{Relay}} = \frac{V_{CC} - V_{CE0}}{\text{max}} \quad , \quad \text{where } V_{CE0} = 0V$$

(WORST case)

$$= 24 - 0$$

$$= 24V$$

$$\therefore I_{\text{Relay}} = \frac{V_{\text{Relay}}}{R_{\text{Relay}}} = \frac{24V}{96\Omega} (A) = 0.25A \quad (\text{or } 250mA)$$

(max.)

For switching processes, derate β by some factor,
e.g. 90%, 50% etc...

$$\text{i.e. } \beta_{\text{SWITCH}} = \frac{500}{10} = 50$$

(this is done to guarantee that switching does happen).

$$\therefore I_B = \frac{I_C}{\beta_{\text{SWITCH}}} = \frac{250}{50} = 5mA$$

$$\therefore R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{24 - 0.7V}{5 \text{ mA}} (K)$$

(See previous question on KVL (A))

$$= 4.66K\Omega$$

Use 4.7K standard.

(b) Missing EMF protection diode.

⇒ Transistor will damage as switching.
Add the diode

