

1.1)

(i)

$$V_{CC} = I_A R_A + I_B R_B + V_{BE} \quad \text{--- (1)}$$

$$\text{Maar } I_A = I_B + I_C \quad \text{--- (2)}$$

$$\text{en } I_C = \beta I_B \quad \text{--- (3)}$$

Met (2) en (3) volgt dat:

$$I_A = I_B (1 + \beta) \quad \text{--- (4)}$$

Stel in (1) dan volgt:

$$V_{CC} = I_B (1 + \beta) R_A + I_B R_B + V_{BE}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{(1 + \beta) R_A + R_B}$$

$$= \frac{20\text{V} - 0,7\text{V}}{(1 + 120) \cdot 4,7\text{k}\Omega + 680\text{k}\Omega}$$

$$= 15,46 \mu\text{A}$$

[5]

(ii)

$$V_{CC} = I_A R_A + V_{CE} \quad \text{--- (1)}$$

$$\Rightarrow V_{CE} = V_{CC} - I_A R_A$$

$$= V_{CC} - I_B (1 + \beta) R_A$$

~~iii)~~ (iii) Verwijder de gelijpennig,
$$= 11,208 \text{ V}$$
 [2]

1.2

$$(i) \quad V_{CC} = I_{\text{motor}} \cdot R_{\text{motor}} + V_{CE} \checkmark$$

* Os skakelaar S toe is, is transistor walaan
 $\Rightarrow V_{CE} = 0V \checkmark$

$$\begin{aligned} \Rightarrow I_{\text{motor}} &= \frac{V_{CC}}{R_{\text{motor}}} \\ &= \frac{24V}{120\Omega} \\ &= 200 \text{ mA} \checkmark \end{aligned}$$

* Vir skakel met 'n transistor word $\beta_S = \frac{\beta}{10}$ gedefinieer.

$$\begin{aligned} \beta_S &= \frac{50}{10} \\ &= 5 \end{aligned}$$

$$\text{Dus } I_B = \frac{I_C}{\beta_S} \checkmark$$

$$\text{Waar } I_C = I_{\text{motor}}$$

$$\begin{aligned} \Rightarrow I_B &= \frac{200 \text{ mA}}{5} \\ &= 40 \text{ mA} \checkmark \end{aligned}$$

$$\text{* Nou } V_{CC} = I_B R_B + V_{BE} \checkmark$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$= \frac{24V - 0,7V}{40 \text{ mA}}$$


$$= 582,5 \Omega \checkmark$$

[8]

(ii) Die diode beheert de transistors
 kan die hoge spanning niet ontsteken in
 die mindere van die motor en die stroom
 afgeleidel wordt!

[2]

2.1

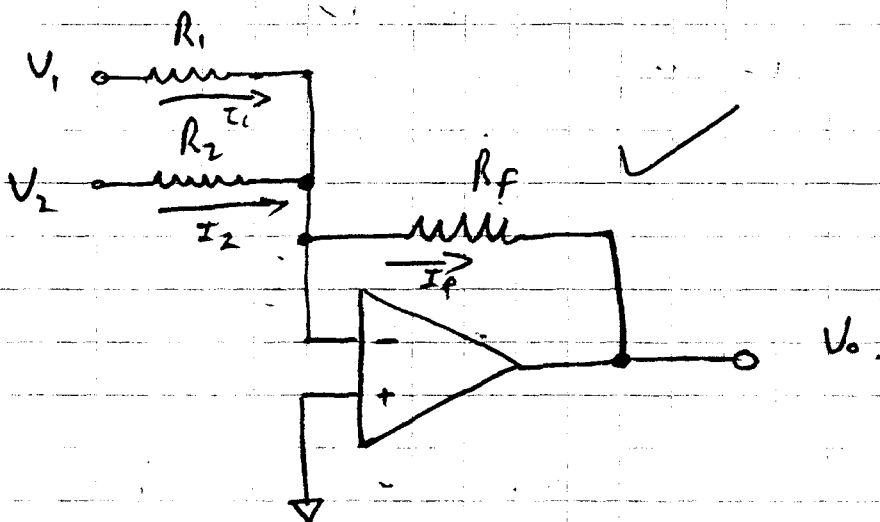

→ Dit is in frequentie afname daarom is.

$$V_+ \approx V_- \quad V_+ = 0V \quad \checkmark \text{ grondverbinding}$$

$$\Rightarrow V_- = 0V.$$

Nou $I_1 + I_2 = I_f$ \checkmark geen stroom in het by V_-
 in groot ingang ingesloten.

$$\text{Nou } I_1 = \frac{V_1 - V_-}{R_1} = \frac{V_1}{R_1} \quad \checkmark$$

$$\text{en } I_2 = \frac{V_2 - V_-}{R_2} = \frac{V_2}{R_2}$$


$$\text{en } I_f = \frac{V_o - V_-}{R_f} = -\frac{V_o}{R_f} \quad \checkmark$$

$$\text{Dus is } \frac{V_1}{R_1} + \frac{V_2}{R_1} = \frac{-V_0}{R_f}$$

$$\Rightarrow V_0 = \frac{-R_f}{R} (V_1 + V_2) \checkmark$$

$$\text{indeel } R_1 = R_2 = R$$

[7]

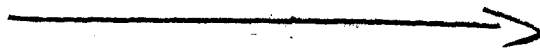

2.2

• Dit is in terug naar stroombron

$$\Rightarrow V_+ = V_- \checkmark$$

$$\begin{aligned} \text{Nu } V_+ &= \frac{4 \text{ k}\Omega}{(4 \text{ k}\Omega + 6 \text{ k}\Omega)} \times 5 \text{ V} \\ &= 2 \text{ V} \end{aligned} \checkmark$$

$$\Rightarrow V_- = 2 \text{ V} \checkmark$$

- Die stroom door die $3 \text{ k}\Omega$ weerstand

$$I_3 = \frac{5 \text{ V} - V_-}{3 \text{ k}\Omega}$$

$$= \frac{5 \text{ V} - 2 \text{ V}}{3 \text{ k}\Omega} = 1 \text{ mA} \checkmark$$

- Die stroom door die $12 \text{ k}\Omega$ weerstand is gelijk aan die stroom door die $3 \text{ k}\Omega$.


$$I_3 = I_{12} \checkmark$$

$$\text{Now } I_{12} = \frac{V_- - V_o}{12 \text{ k}\Omega} \checkmark$$

$$\begin{aligned} \Rightarrow V_o &= V_- - I_{12} \times 12 \text{ k}\Omega \\ &= 2 \text{ V} - (1 \text{ mA} \times 12 \text{ k}\Omega) \end{aligned}$$


$$V_o = -10 \text{ V} \checkmark$$

[7]

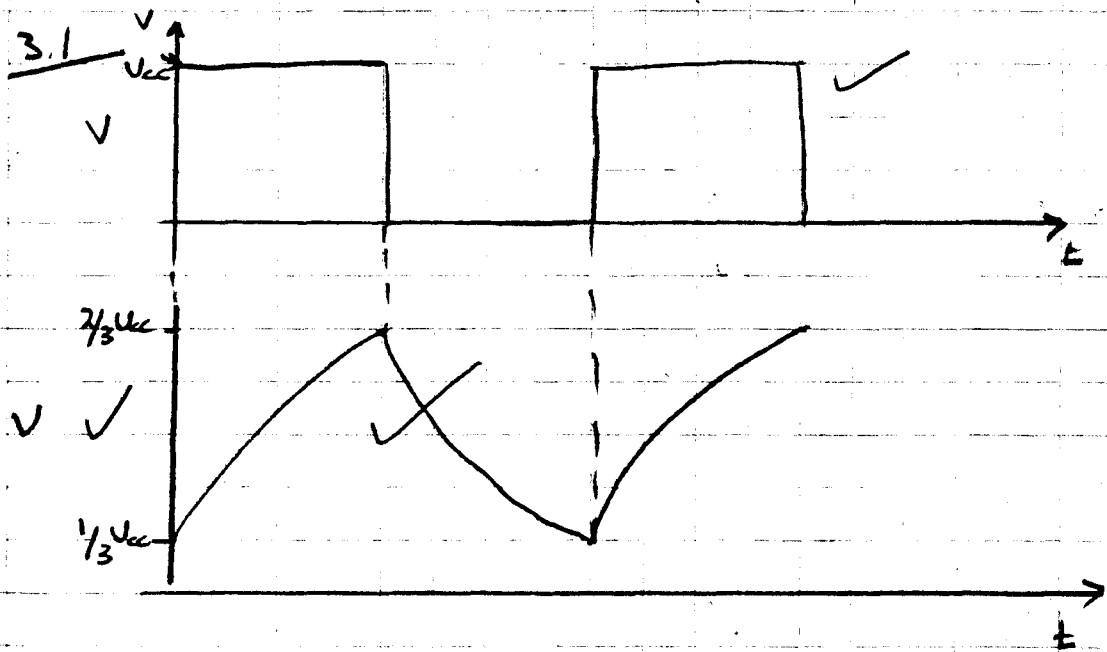

[3]

3.2

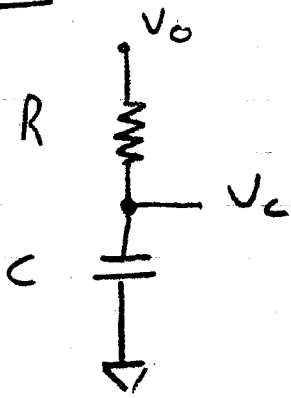

Now $V_o = Ri + V_c$ ✓

Major $i = \frac{dq}{dt}$ ✓ def.

an $q = C V_c$ ✓ def

$$\frac{dq}{dt} = C \frac{dV_c}{dt}$$

$$\Rightarrow V_o = RC \frac{dV_c}{dt} + V_c$$

$$\Rightarrow \frac{1}{RC} \int_{t_1}^{t_2} dt = \int_{V_1}^{V_2} \frac{dV_c}{V_o - V_c}$$
 ✓

$$\Rightarrow [t]_{t_1}^{t_2} = RC [-\ln(V_o - V_c)]_{V_1}^{V_2}$$

Now in die Strom out here die kapazitor
2R.

$$\Rightarrow \Delta t = 2RC \ln \left[\frac{V_{cc} - \frac{1}{3}V_{cc}}{V_{cc} - \frac{2}{3}V_{cc}} \right]$$

$$= 2RC \ln(2)$$

$$= RC (1.386 \dots)$$
 ✓

[6]

4.1

$$\frac{53}{2} = 26 \rightarrow 1$$

$$\frac{26}{2} = 13 \rightarrow 0$$

$$\frac{13}{2} = 6 \rightarrow 1$$

$$\frac{6}{2} = 3 \rightarrow 0$$

$$\frac{3}{2} = 1 \rightarrow 1$$

$$\frac{1}{2} = 0 \rightarrow 1$$

$$53_{\text{Dec}} \rightarrow 110101_{\text{Bin}} \quad \checkmark$$

$$AE8 = A \times 16^2 + E \times 16^1 + 8 \times 16^0$$

$$= 10 \times 16^2 + 14 \times 16^1 + 8 \times 16^0$$

$$= 2792. \quad \checkmark$$



[2]

4.2.

$$F = \overline{\overline{A.A} . \overline{B.B} . \overline{A.A} . \overline{B.B}}$$

$$= \overline{\overline{A} . \overline{B} . \overline{A} . \overline{B}}$$

$$= \overline{A+B} . \overline{A+B}$$

$$= (A+B) . (A+B)$$

$$= (\overline{A+B}) + (\overline{A+B})$$

$$F = \overline{A+B}$$

$$(A.A = A)$$

$$\overline{A} . \overline{B} = \overline{A+B}$$

$$(\overline{\overline{A}} = A)$$

$$\overline{A.B} \neq \overline{A} + \overline{B}$$

$$A+A = A$$

[4]

4.3

$$F = \overline{A.D + \overline{B}.C + D}$$


$$= \overline{D(A+1) + \overline{B}.C}$$

$$= \overline{D + \overline{B}.C}$$

$$= \overline{D} + \overline{\overline{B}.C}$$

$$= \overline{D} + \overline{\overline{B}} + \overline{C}$$

$$= \overline{D} + B + C$$

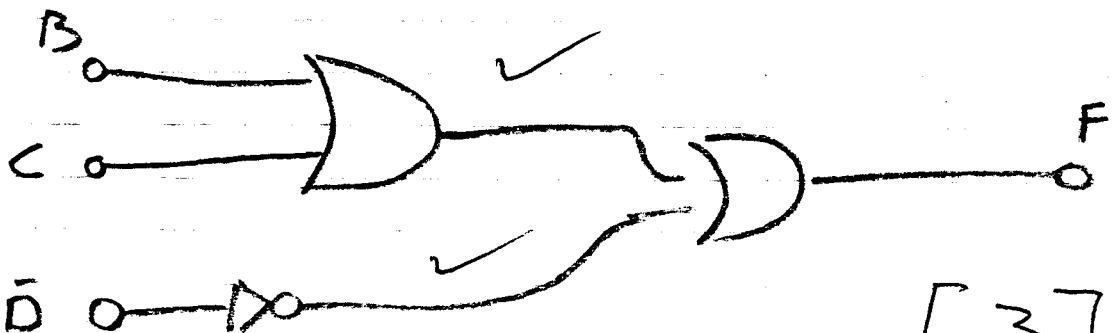

[3]